

# *Physics 212*

## *Lecture 10*

Today's Concept:


Kirchhoff's Rules

# Last Time
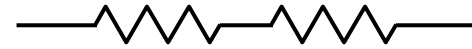
## Resistors in series:

Current through is same.

Voltage drop across each resistor  $i$  is  $IR_i$




$$R_{\text{effective}} = R_1 + R_2$$

## Resistors in parallel:


Voltage drop across is same.

Current through is  $V/R_i$

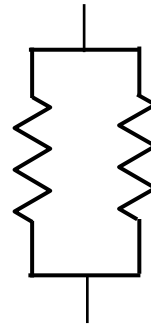


$$\frac{1}{R_{\text{effective}}} = \frac{1}{R_1} + \frac{1}{R_2}$$


## Solved Circuits

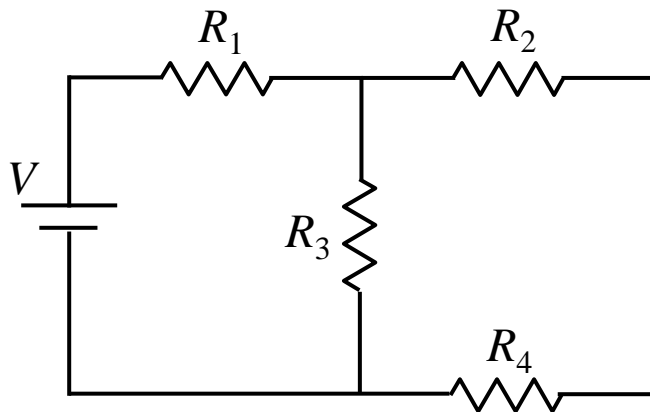


=

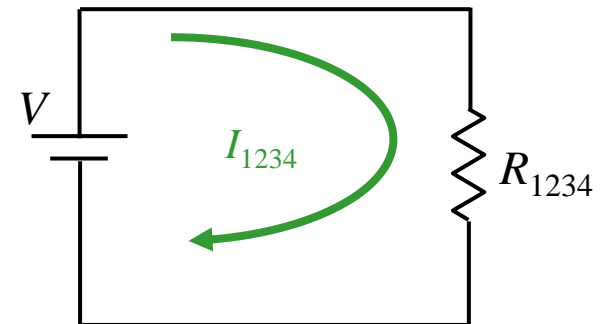

# New Circuit

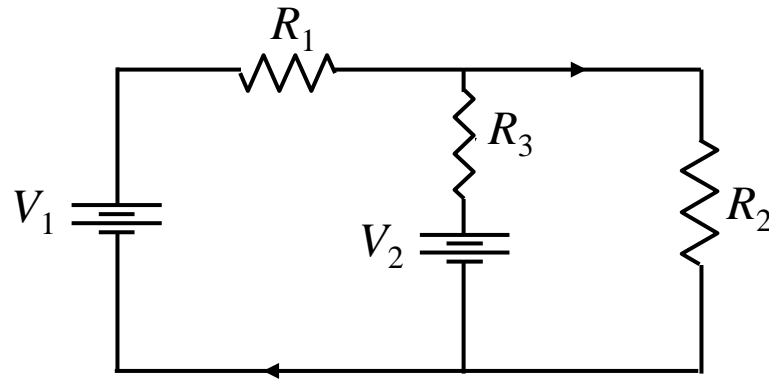

How Can We Solve This One?

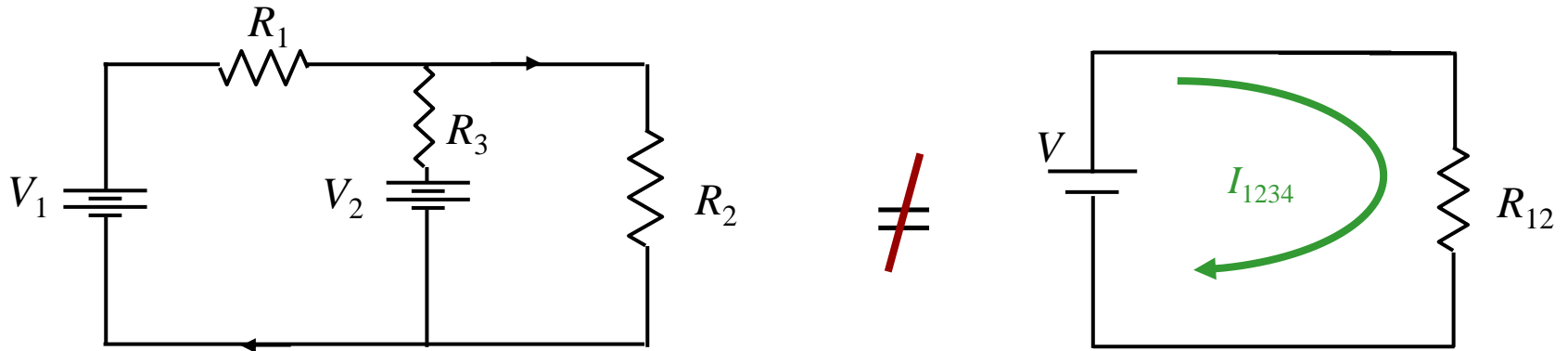


THE ANSWER: Kirchhoff's Rules
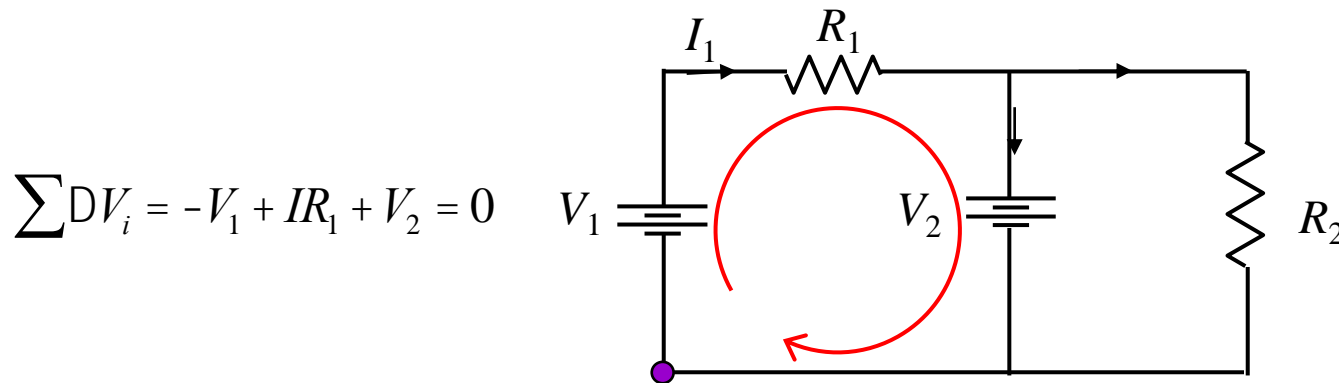
# Kirchhoff's Voltage Rule

$$\sum \Delta V_i = 0$$

Kirchhoff's Voltage Rule states that the sum of the voltage changes caused by any elements (like wires, batteries, and resistors) around a circuit must be zero.




WHY?

The potential difference between a point and itself is zero!
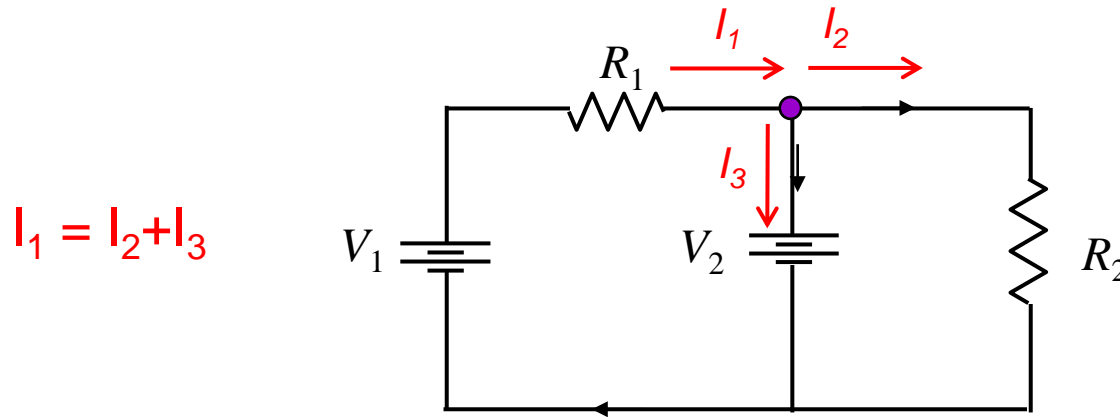
# Kirchhoff's Current Rule

$$\sum I_{in} = \sum I_{out}$$

Kirchhoff's Current Rule states that the sum of all currents entering any given point in a circuit must equal the sum of all currents leaving the same point.



WHY?

Electric Charge is Conserved

# Applying Kirchhoff's Laws in 5 easy steps

## 1) Label all currents

Choose any direction

## 2) Label +/– for all elements

Current goes  $+\Rightarrow -$  (for resistors)  
Long side is + for battery

## 3) Choose loop and direction


Must start on wire, not element.

## 4) Write down voltage drops

First sign you hit is sign to use.
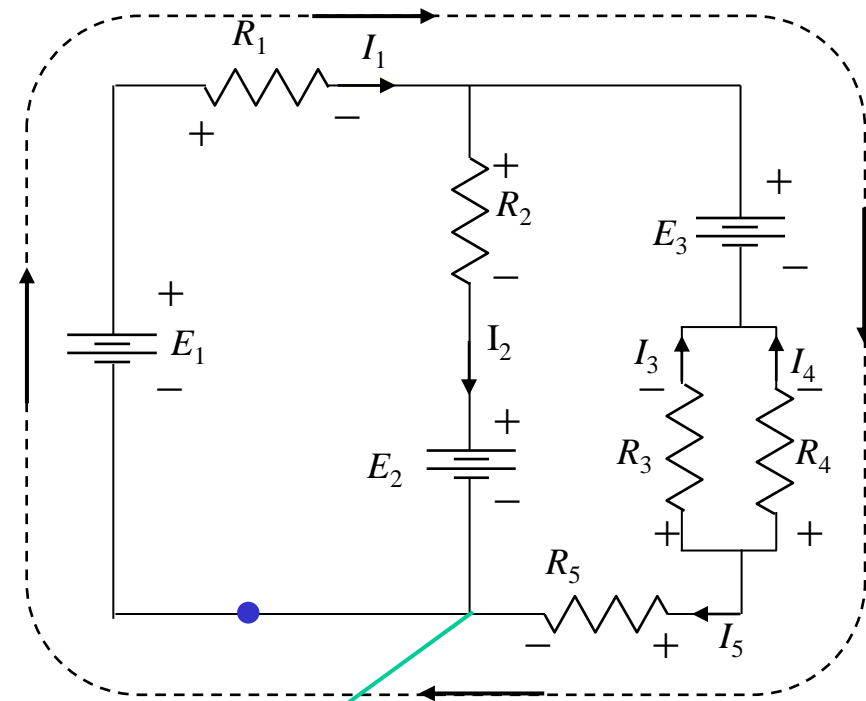
## 5) Write down node equation $I_{\text{in}} = I_{\text{out}}$

$$-E_1 + I_1 R_1 + E_3 - I_4 R_4 + I_5 R_5 = 0$$




$$I_2 + I_5 = I_1$$
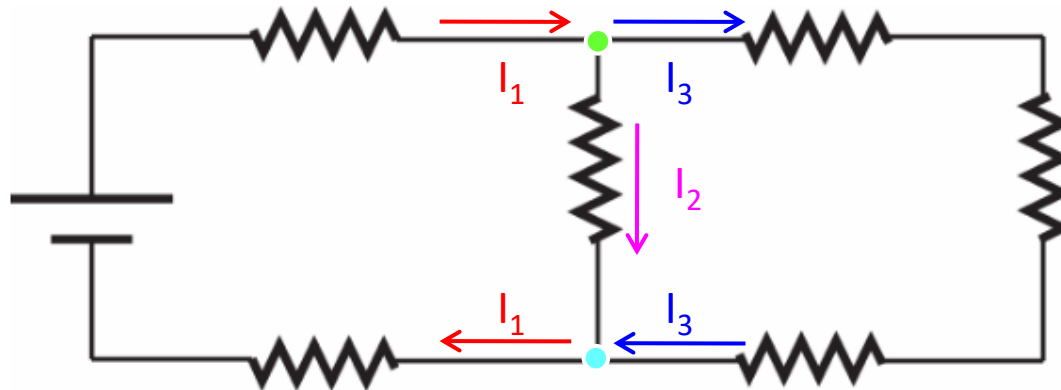
# Check Point 1



How many potentially different currents are there in the circuit shown?



- A. 3      B. 4      C. 5      D. 6      E. 7

Look at the nodes!

**Top node:**  $I_1$  flows in,  $I_2$  and  $I_3$  flow out


**Bottom node:**  $I_2$  and  $I_3$  flow in,  $I_1$  flows out

That's all of them!
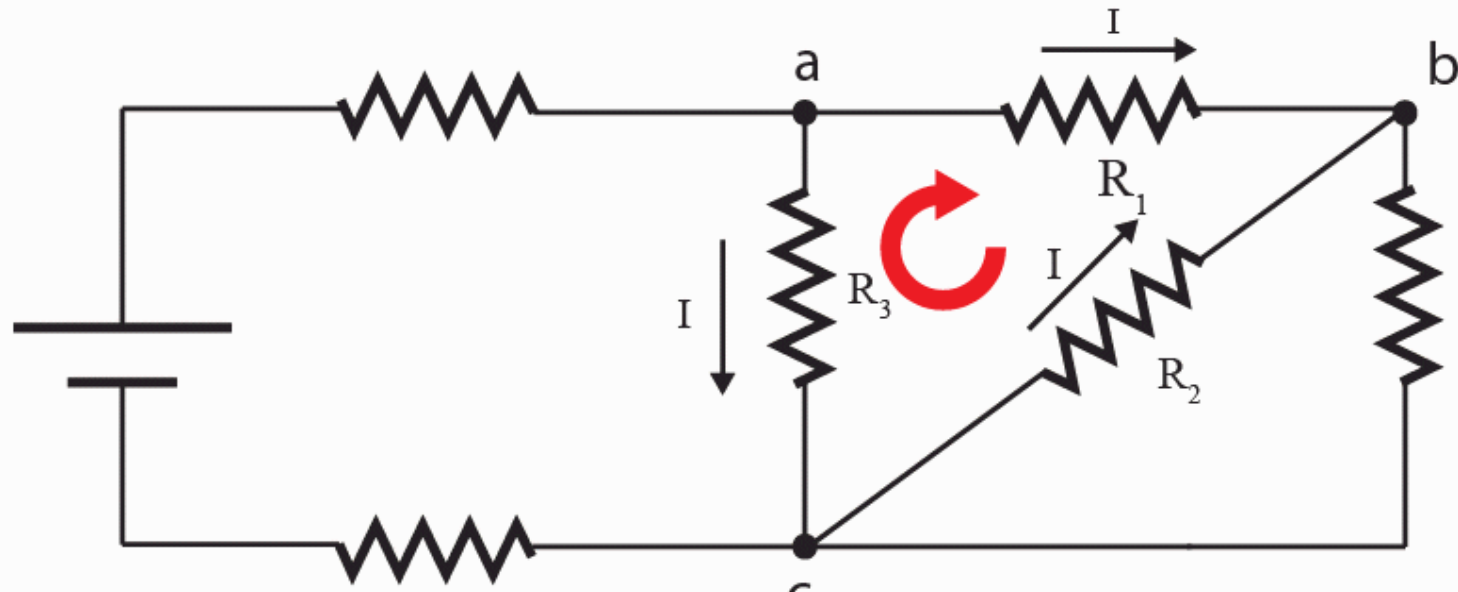
# Check Point 2



In the following circuit, consider the loop abc. The direction of the current through each resistor is indicated by black arrows.



If we are to write Kirchhoff's voltage equation for this loop in the clockwise direction starting from point a, what is the correct order of voltage gains/drops that we will encounter for resistors R1, R2 and R3?

**A.** drop, drop, drop

**B.** gain, gain, gain

**C.** drop, gain, gain

**D.** gain, drop, drop



**E.** drop, drop, gain

With the current  VOLTAGE DROP


Against the current  VOLTAGE GAIN



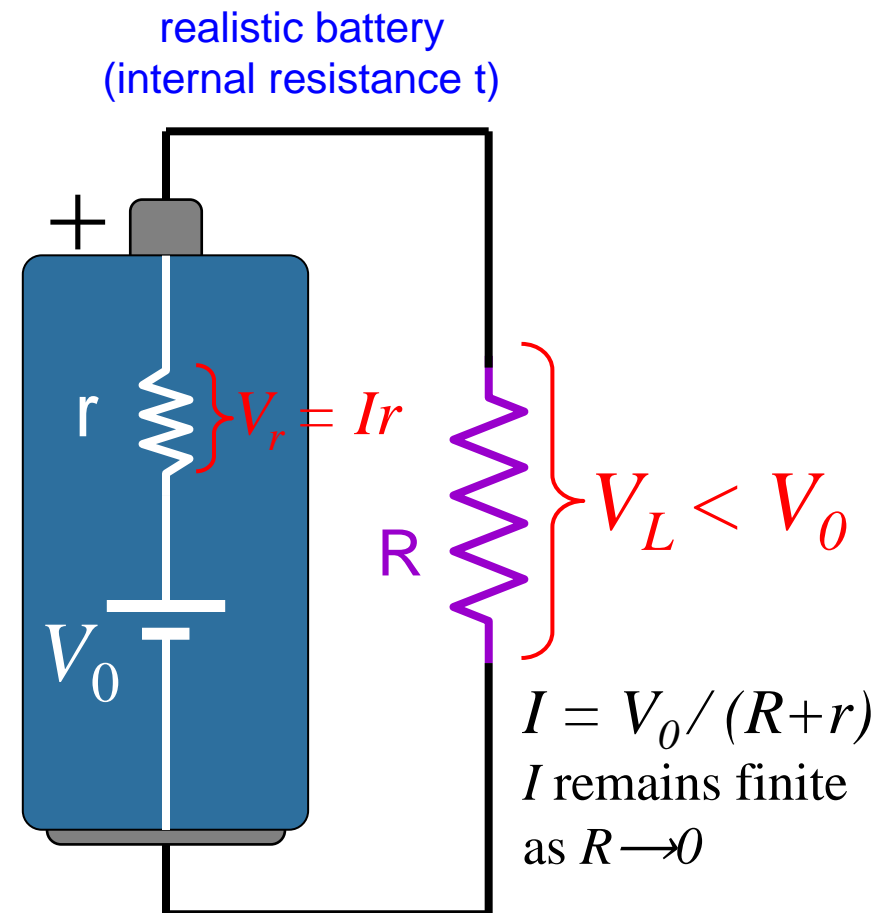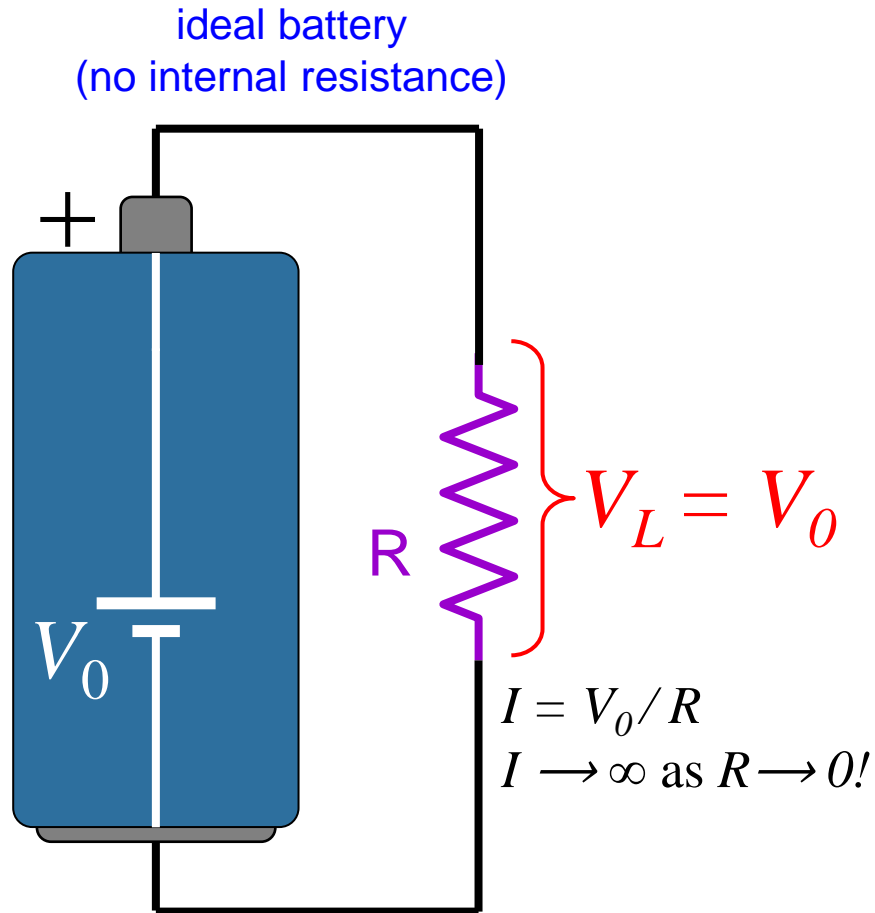
# Model for Real Battery: Internal Resistance



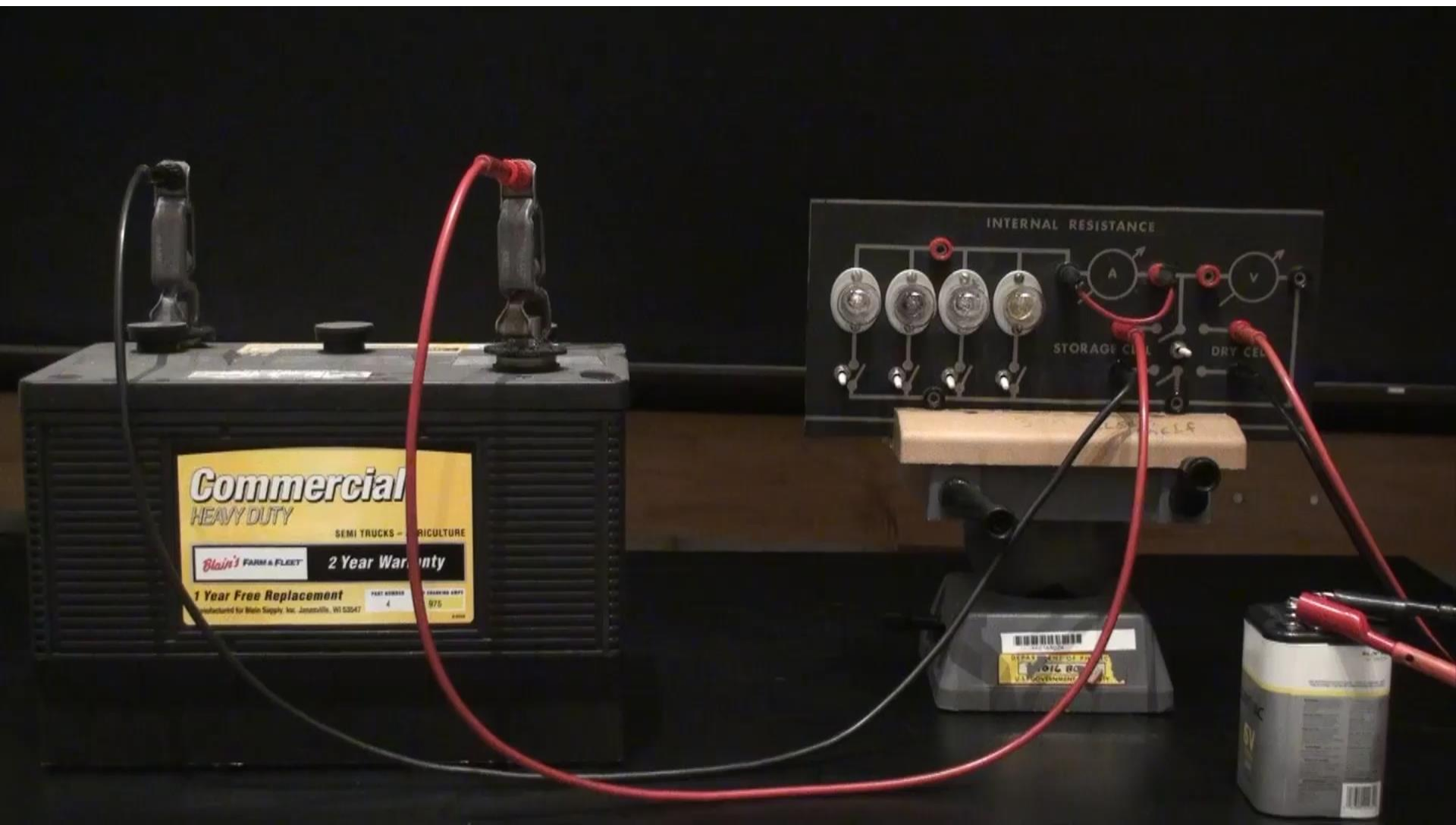Usually, can't supply too much current to the load  
without voltage "sagging"



# Calculation

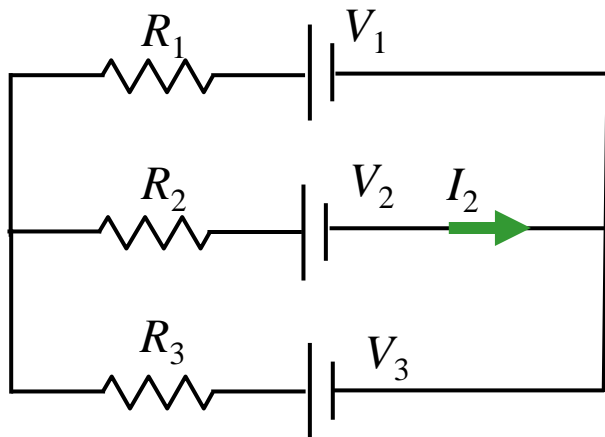

In this circuit, we are given the resistances and battery voltages and are asked to calculate the current through resistor 2.


## Conceptual Analysis:

- Circuit behavior described by Kirchhoff's Rules:
  - KVR:  $\sum V_{drops} = 0$
  - KCR:  $\sum I_{in} = \sum I_{out}$

## Strategic Analysis

- Write down Loop Equations (KVR)
- Write down Node Equations (KCR)
- Solve

# Calculation

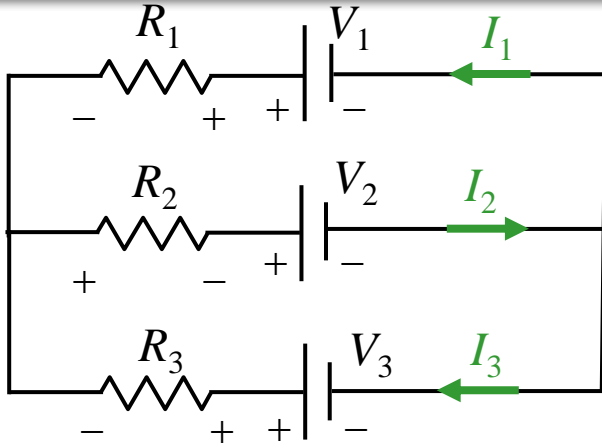

In this circuit, assume  $V_i$  and  $R_i$  are known.


What is  $I_2$  ?

- 1) Label and pick directions for each current
- 2) Label the  $+$  and  $-$  side of each element

This is easy for batteries Long side is  $+$


For resistors, the “upstream” side is  $+$

Now write down loop and node equations

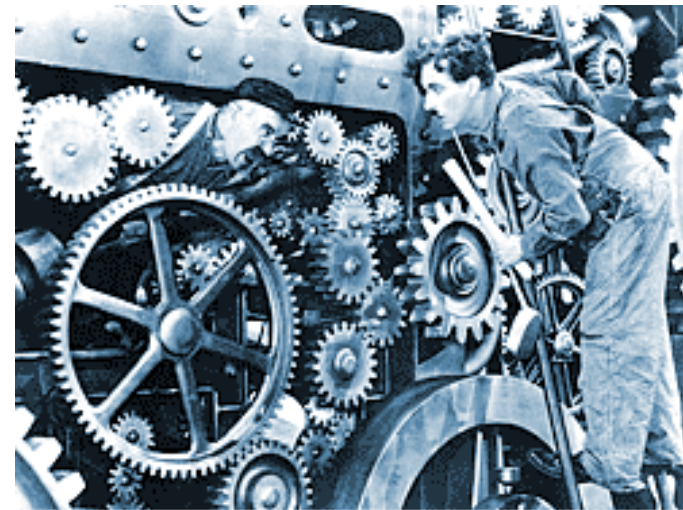

**Just turn the crank.**

# Calculation

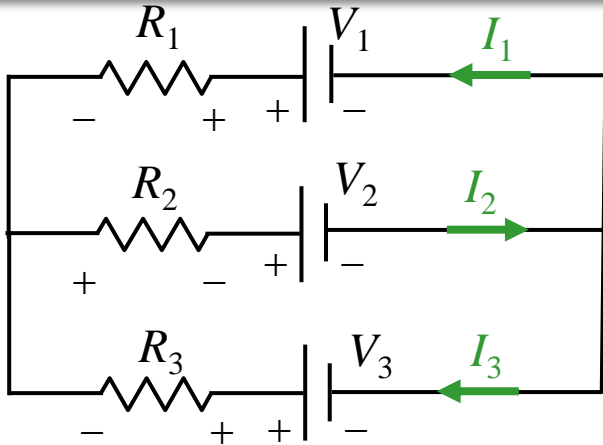

In this circuit, assume  $V_i$  and  $R_i$  are known.

What is  $I_2$  ?

How many equations do we need to write down in order to solve for  $I_2$ ?


- A) 1      B) 2      C) 3      D) 4      E) 5

Why?

- We have 3 unknowns:  $I_1$ ,  $I_2$ , and  $I_3$
- We need 3 independent equations to solve for these unknowns

3) Choose Loops and Directions

# Calculation

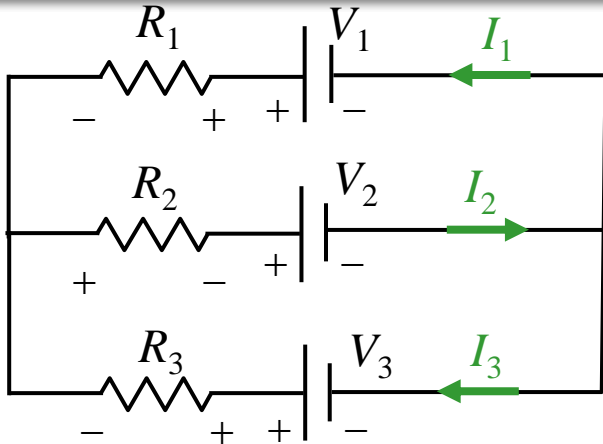

In this circuit, assume  $V_i$  and  $R_i$  are known.

What is  $I_2$  ?

Which of the following equations is NOT correct?

- A)  $I_2 = I_1 + I_3$
- B)  $-V_1 + I_1 R_1 - I_3 R_3 + V_3 = 0$
- C)  $-V_3 + I_3 R_3 + I_2 R_2 + V_2 = 0$
- D)  $-V_2 - I_2 R_2 + I_1 R_1 + V_1 = 0$


4) Write down voltage drops

5) Write down node equation

Why?

- (D) is an attempt to write down *KVR* for the top loop
- Start at negative terminal of  $V_2$  and go clockwise  
 $V_{\text{gain}} (-V_2)$  then  $V_{\text{gain}} (-I_2 R_2)$  then  $V_{\text{gain}} (-I_1 R_1)$  then  $V_{\text{drop}} (+V_1)$

# Calculation

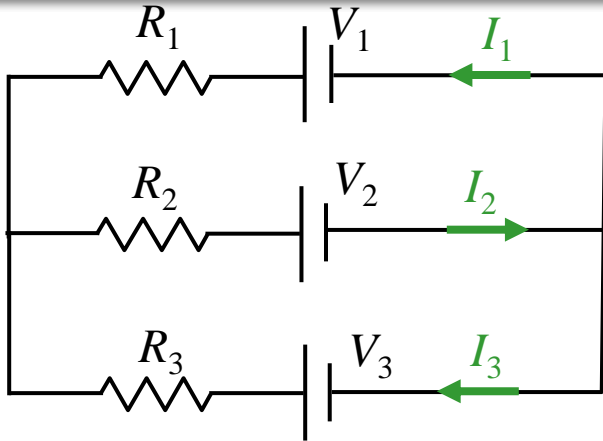

In this circuit, assume  $V_i$  and  $R_i$  are known.

What is  $I_2$  ?

We need 3 equations:  
Which 3 should we use?


1.  $I_2 = I_1 + I_3$
2.  $-V_1 + I_1 R_1 - I_3 R_3 + V_3 = 0$
3.  $-V_3 + I_3 R_3 + I_2 R_2 + V_2 = 0$
4.  $-V_2 - I_2 R_2 - I_1 R_1 + V_1 = 0$

- A) Any 3 will do  
B) 1, 2, and 4  
C) 2, 3, and 4

Why?

- We need 3 INDEPENDENT equations
- Equations 2, 3, and 4 are NOT INDEPENDENT  
 $\text{Eqn 2} + \text{Eqn 3} = -\text{Eqn 4}$
- We must choose Equation 1 and any two of the remaining ( 2, 3, and 4)

# Calculation

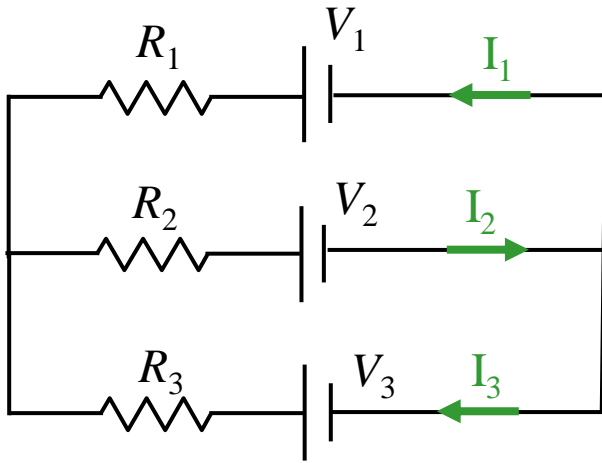

In this circuit, assume  $V_i$  and  $R_i$  are known.

What is  $I_2$  ?

We have 3 equations and 3 unknowns.


$$I_2 = I_1 + I_3$$

$$V_1 + I_1 R_1 - I_3 R_3 + V_3 = 0$$

$$V_2 - I_2 R_2 - I_1 R_1 + V_1 = 0$$



Now just need to solve ☺

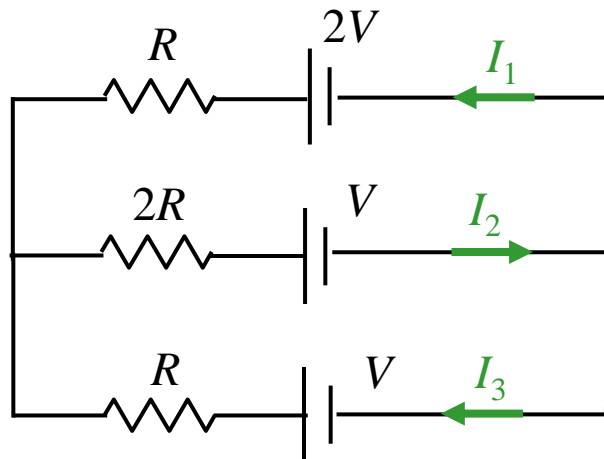

The solution will get very messy!

Simplify: assume  $V_2 = V_3 = V$

$$V_1 = 2V$$

$$R_1 = R_3 = R$$


$$R_2 = 2R$$



# Calculation: Simplify

In this circuit, assume  $V$  and  $R$  are known.

What is  $I_2$  ?

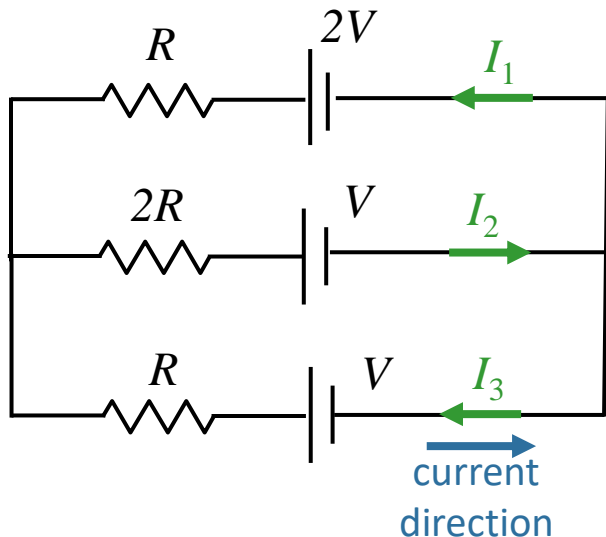

We have 3 equations and 3 unknowns.

$$I_2 = I_1 + I_3$$

$$-2V + I_1 R - I_3 R + V = 0 \quad (\text{outside})$$

$$-V - I_2(2R) - I_1 R + 2V = 0 \quad (\text{top})$$


With this simplification, you can verify:

$$I_2 = (1/5) V/R$$

$$I_1 = (3/5) V/R$$

$$I_3 = (-2/5) V/R$$

# Check Point 3a

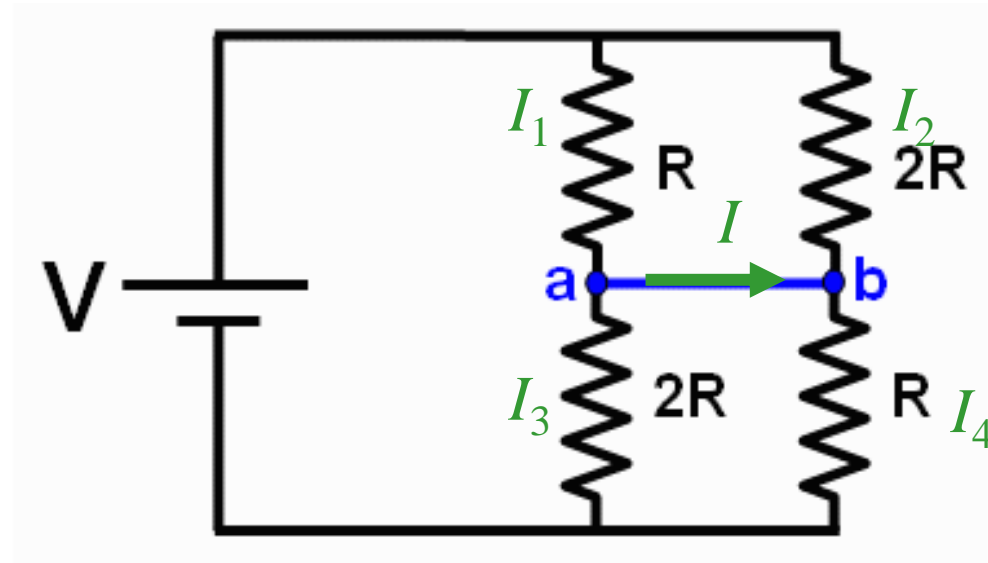

Which of the following best describes the current flowing in the blue wire connecting points **a** and **b**?

- A.** Positive current flows from *a* to *b*      **B.** Positive current flows from *b* to *a*  
**C.** No current flows between *a* and *b*



$$I_1 R - I_2 (2R) = 0 \quad \rightarrow \quad I_2 = \frac{1}{2} I_1$$

$$I_4 R - I_3 (2R) = 0 \quad \rightarrow \quad I_4 = 2 I_3$$

$$I = I_1 - I_3$$

$$I + I_2 = I_4 \quad \rightarrow \quad I_1 - I_3 + \frac{1}{2} I_1 = 2 I_3 \quad \rightarrow \quad I_1 = 2 I_3 \quad \rightarrow \quad I = +I_3$$

## Check point 3b

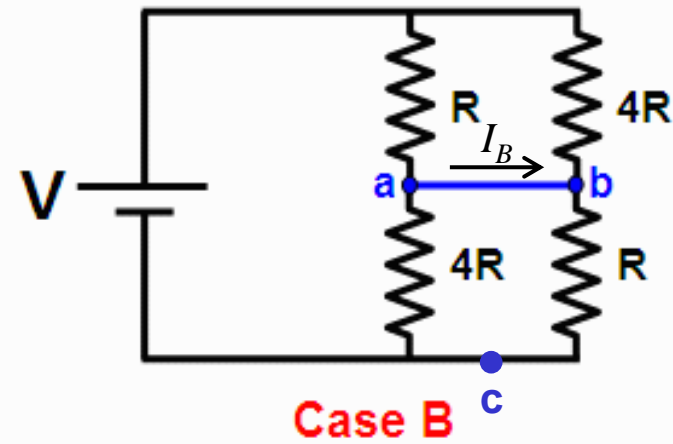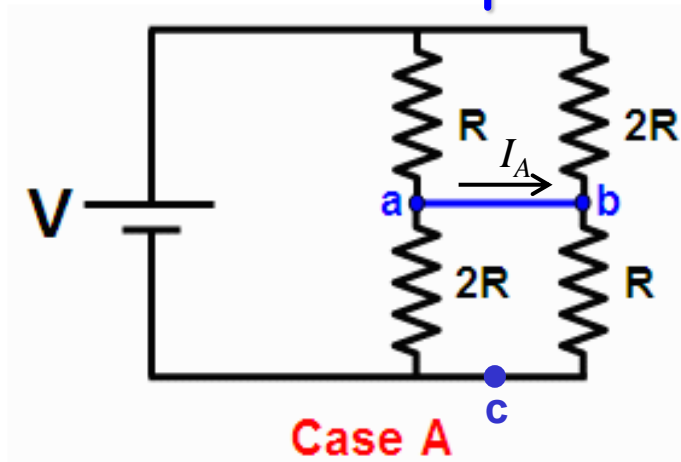

which case is the current flowing in the blue wire connecting points **a** and **b** the largest?

- A.** Case A                      **B.** Case B                      **C.** They are both the same

Current will flow from left to right in both cases.

In both cases,  $V_{ac} = V/2$



$$I_{2R} = 2I_{4R}$$

$$\begin{aligned} I_A &= I_R - I_{2R} \\ &= I_R - 2I_{4R} \end{aligned}$$

$$I_B = I_R - I_{4R}$$

# Summary

## 1) Label all currents

Choose any direction

## 2) Label +/− for all elements

Current goes  $+\Rightarrow -$  (for resistors)  
Long side is + for battery

## 3) Choose loop and direction


Must start on wire, not element.

## 4) Write down voltage drops

First sign you hit is sign to use.
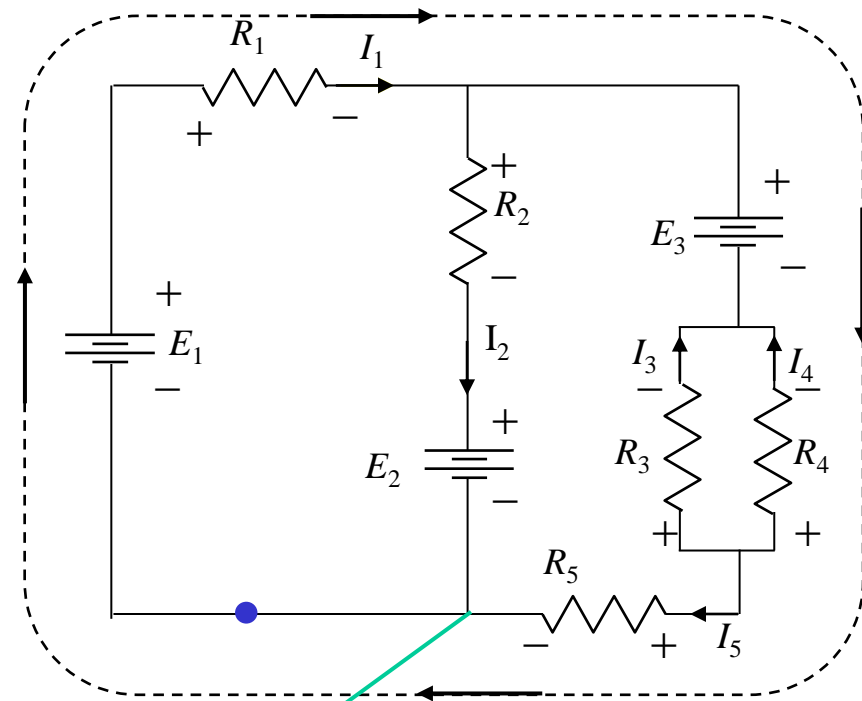
## 5) Write down node equation $I_{\text{in}} = I_{\text{out}}$

$$-E_1 + I_1 R_1 + E_3 - I_4 R_4 + I_5 R_5 = 0$$



$$I_2 + I_5 = I_1$$