

# *Physics 212*

## *Lecture 8*

### Today's Concept:

#### Capacitors

(Capacitors in a circuits, Dielectrics, Energy in capacitors)

So what exactly does capacitance mean? What does a capacitor do in real life?

# Energy in Capacitors (from lect 7)

## Energy Stored in Capacitors

$$U = \frac{1}{2} QV$$

or


$$U = \frac{1}{2} \frac{Q^2}{C}$$

or


$$U = \frac{1}{2} CV^2$$

Energy Density

$$u = \frac{1}{2} \epsilon_0 E^2$$

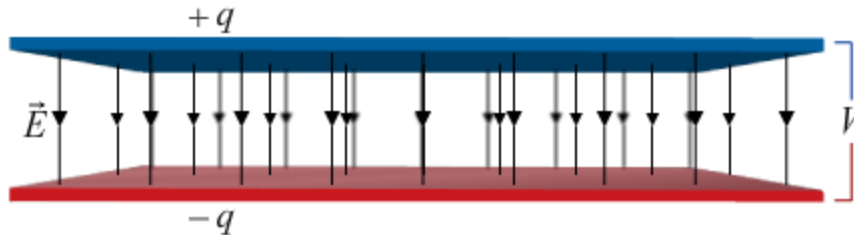


# Simple Capacitor Circuit

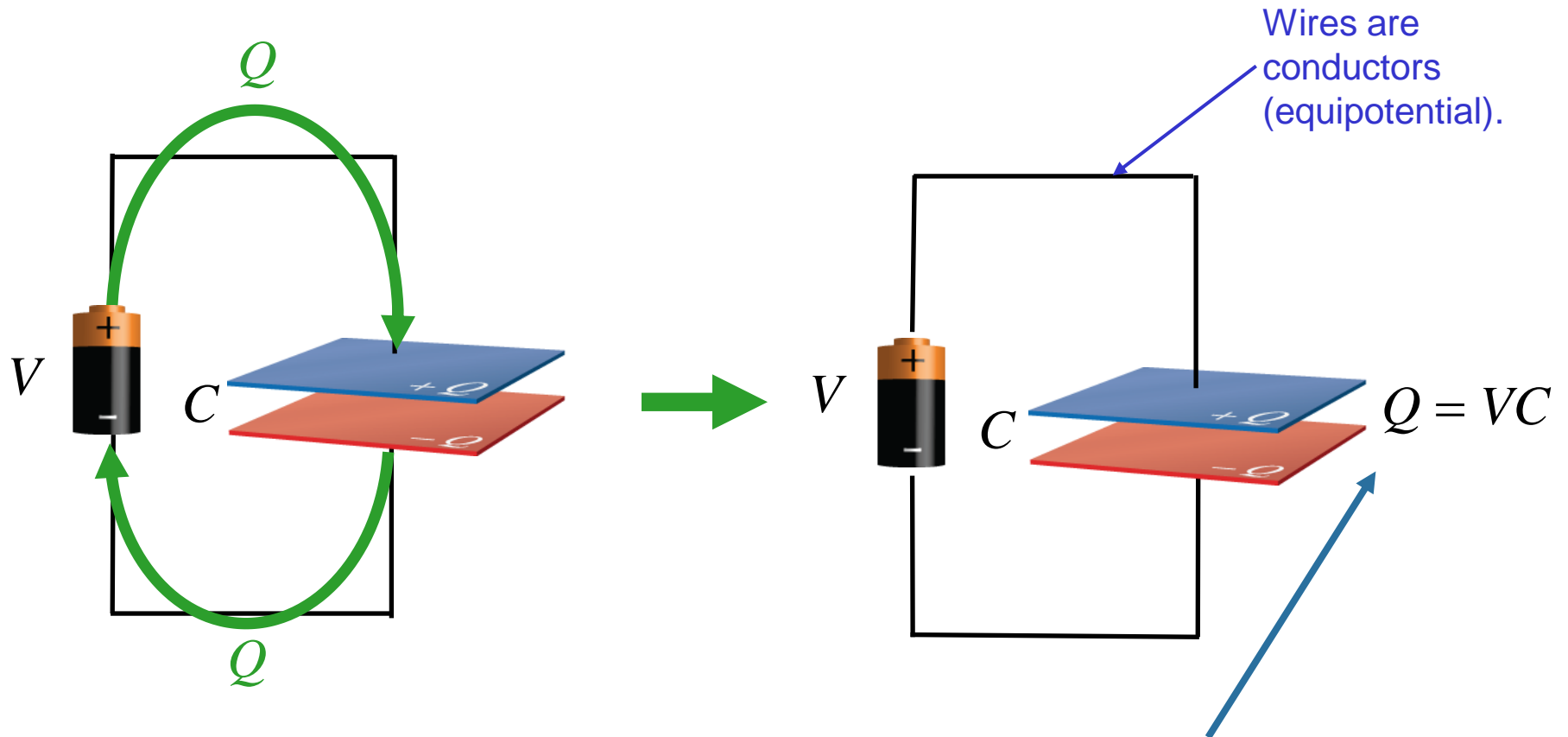

This “ $Q$ ” really means that the battery has moved charge  $Q$  from one plate to the other, so that one plate holds  $+Q$  and the other  $-Q$ .

# Parallel Capacitor Circuit

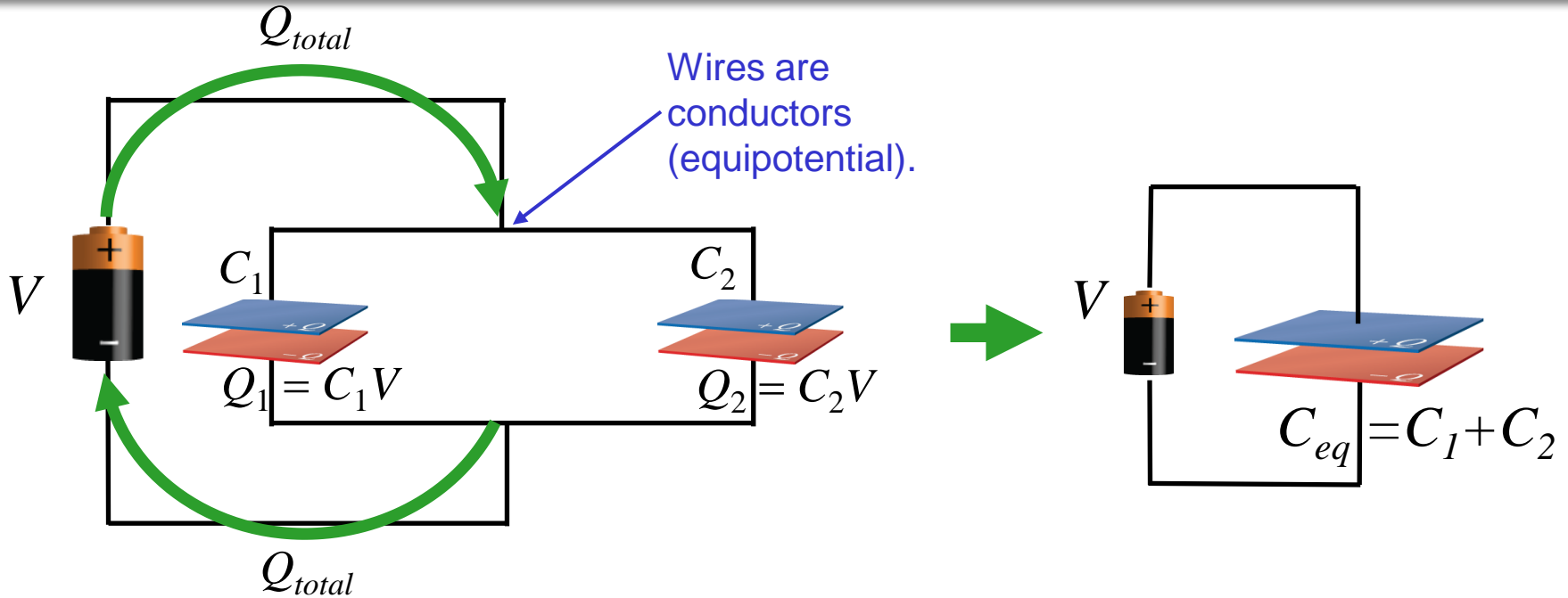


**Key point:**  $V$  is the same for both capacitors

**Key Point:**  $Q_{total} = Q_1 + Q_2 = VC_1 + VC_2 = V(C_1 + C_2)$

$$C_{total} = C_1 + C_2$$

# Series Capacitor Circuit

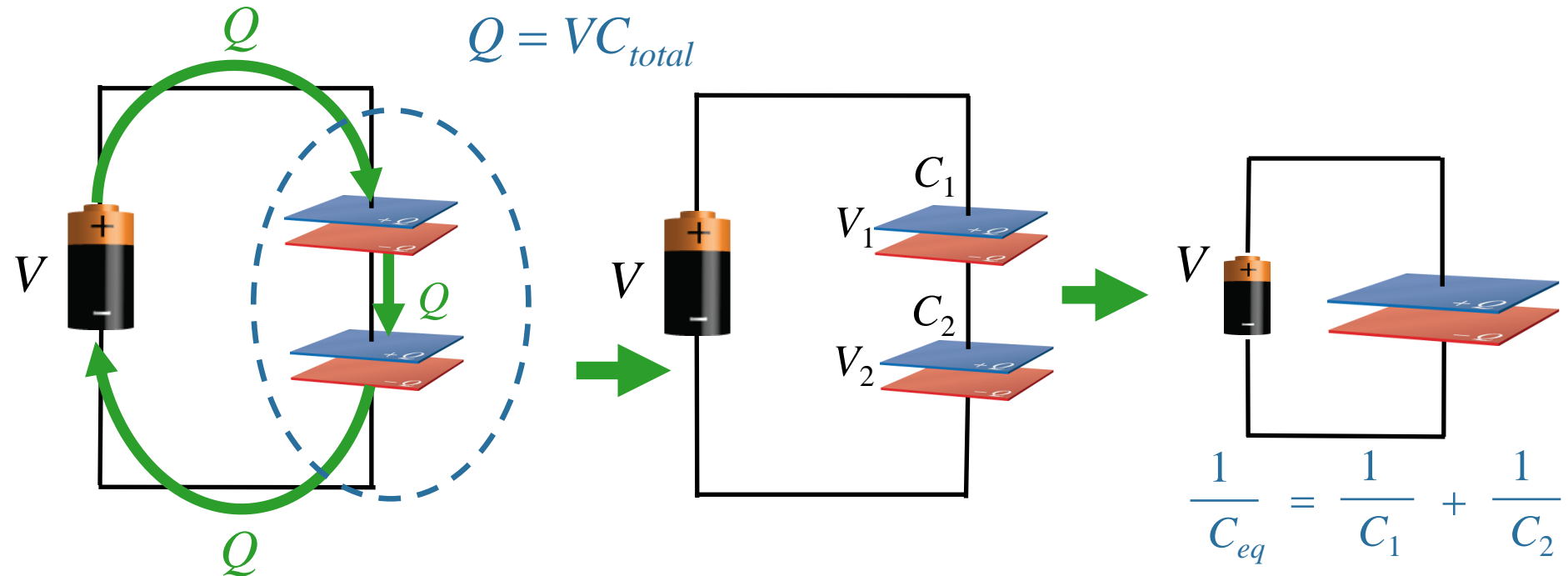

**Key point:**  $Q$  is the same for both capacitors

**Key point:**  $Q = VC_{total} = V_1C_1 = V_2C_2$




**Also:**  $V = V_1 + V_2 \longrightarrow Q/C_{total} = Q/C_1 + Q/C_2$

$$\frac{1}{C_{total}} = \frac{1}{C_1} + \frac{1}{C_2}$$

# Check Point 1



Which has lowest total capacitance:

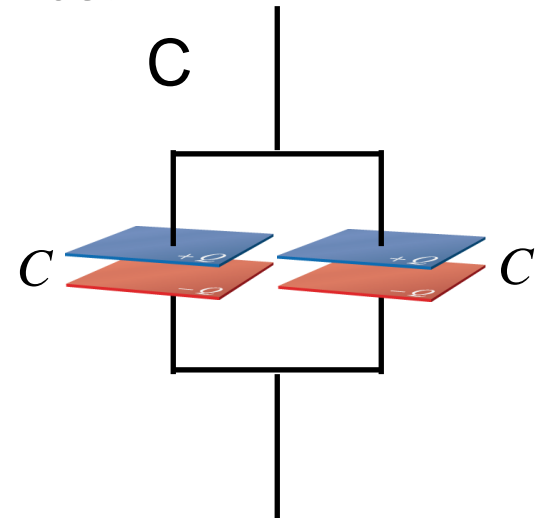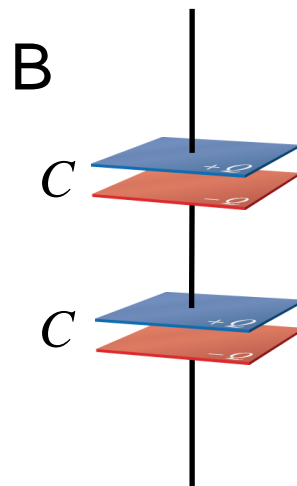
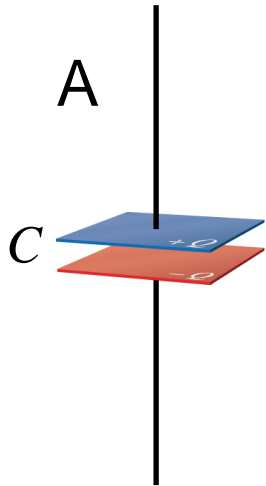


## Check Point 2


Which has lowest total capacitance?

A) Single Capacitor    B) 4 Capacitors    C) Same

:

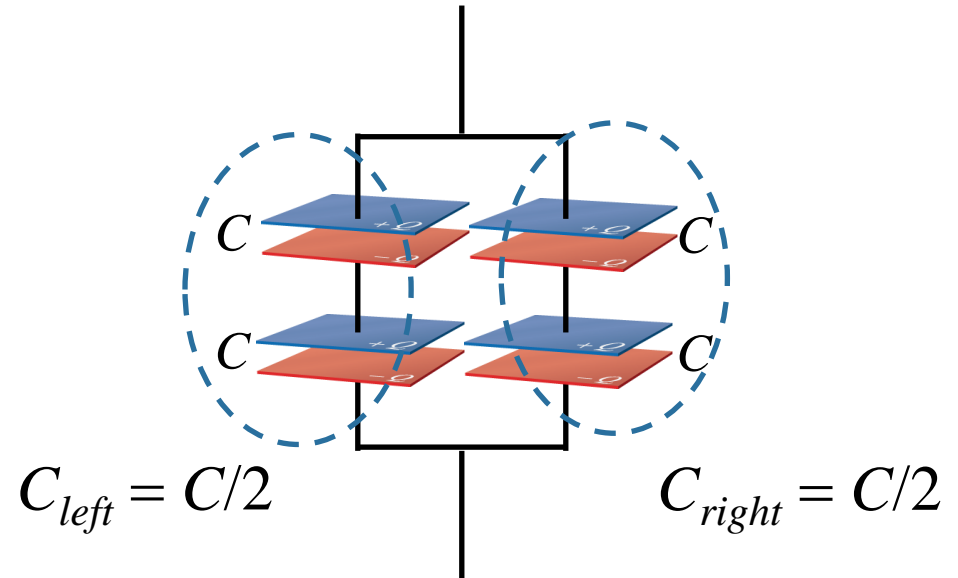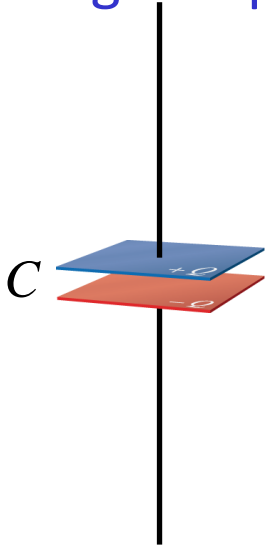

# Similar to CheckPoint 3

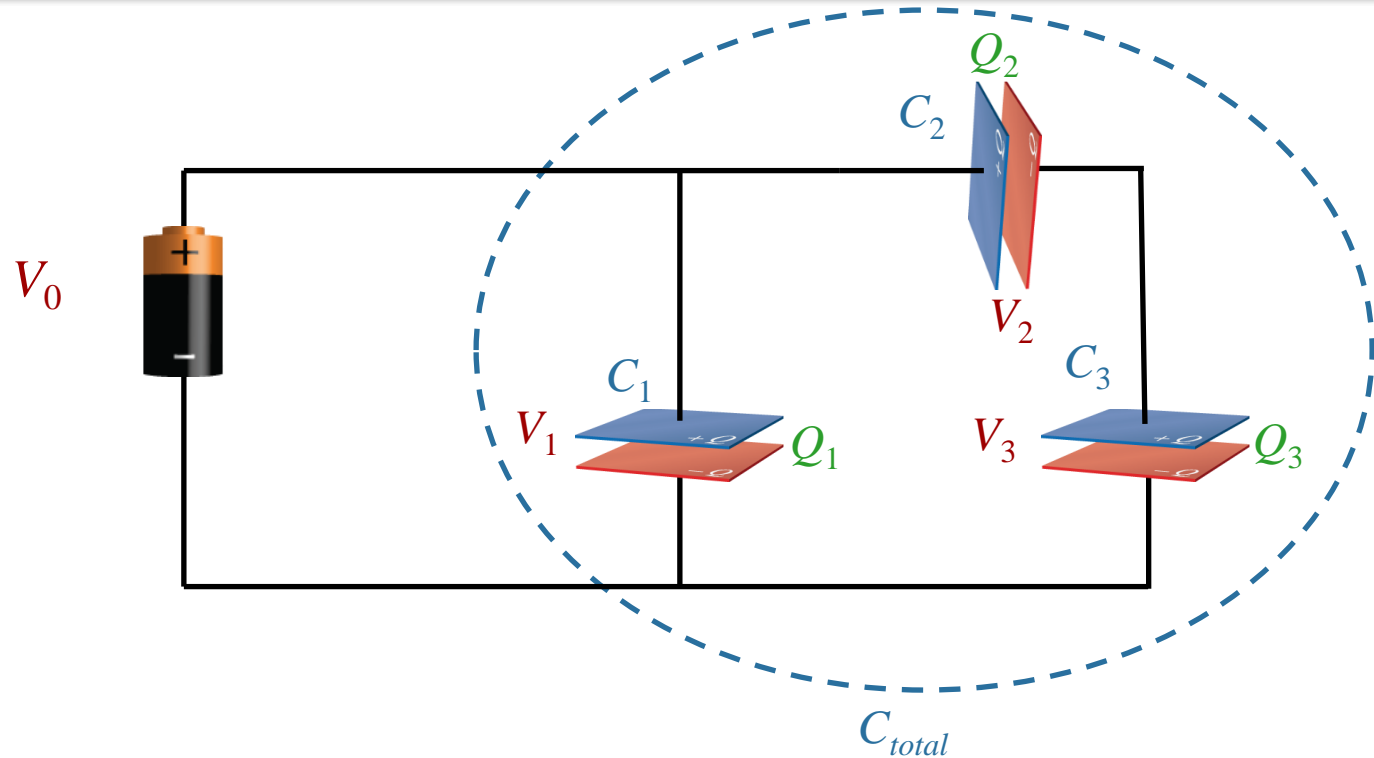

Which of the following is **NOT** necessarily true:



- A)  $V_0 = V_1$
- B)  $C_{total} > C_1$
- C)  $V_2 = V_3$
- D)  $Q_2 = Q_3$
- E)  $V_1 = V_2 + V_3$


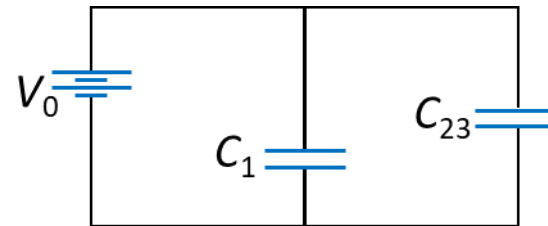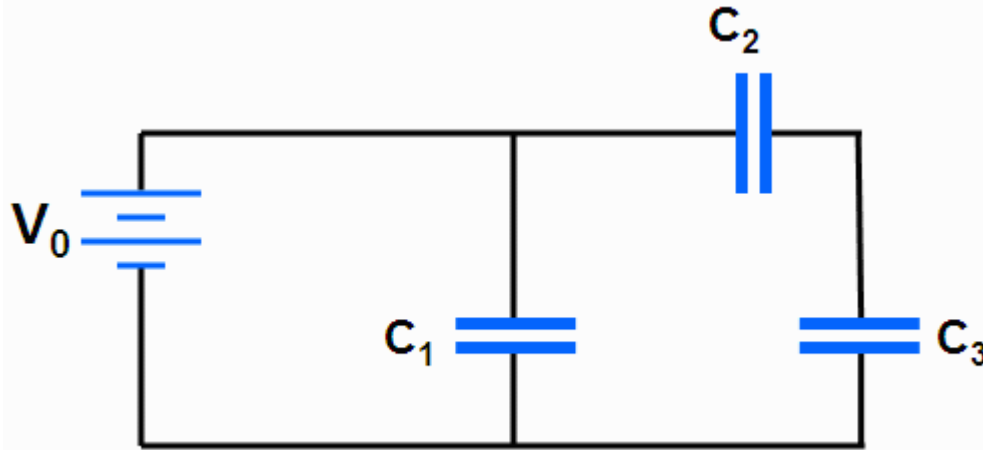
# Check Point 3



A circuit consists of three unequal capacitors  $C_1$ ,  $C_2$ , and  $C_3$  which are connected to a battery of voltage  $V_0$ . The capacitance of  $C_2$  is twice that of  $C_1$ . The capacitance of  $C_3$  is three times that of  $C_1$ . The capacitors obtain charges  $Q_1$ ,  $Q_2$ , and  $Q_3$ .



~~A.~~  $Q_1 > Q_3 > Q_2$  ~~B.~~  $Q_1 > Q_2 > Q_3$  **C.**  $Q_1 > Q_2 = Q_3$  **D.**  $Q_1 = Q_2 = Q_3$  **E.**  $Q_1 < Q_2 = Q_3$

1.  $\therefore Q_2 = Q_3$  (capacitors in series)

2. How about  $Q_1$  vs.  $Q_2$  and  $Q_3$ ? Calculate  $C_{23}$  first.

$$\frac{1}{C_{23}} = \frac{1}{C_2} + \frac{1}{C_3} = \frac{1}{2C_1} + \frac{1}{3C_1} = \frac{5}{6C_1}$$




$$C_{23} = \frac{6}{5}C_1$$



$$Q_1 = C_1 V_0$$

$$Q_{23} = Q_2 = Q_3 = C_{23} V_0 = \frac{6}{5} C_1 V_0$$


# Dielectrics

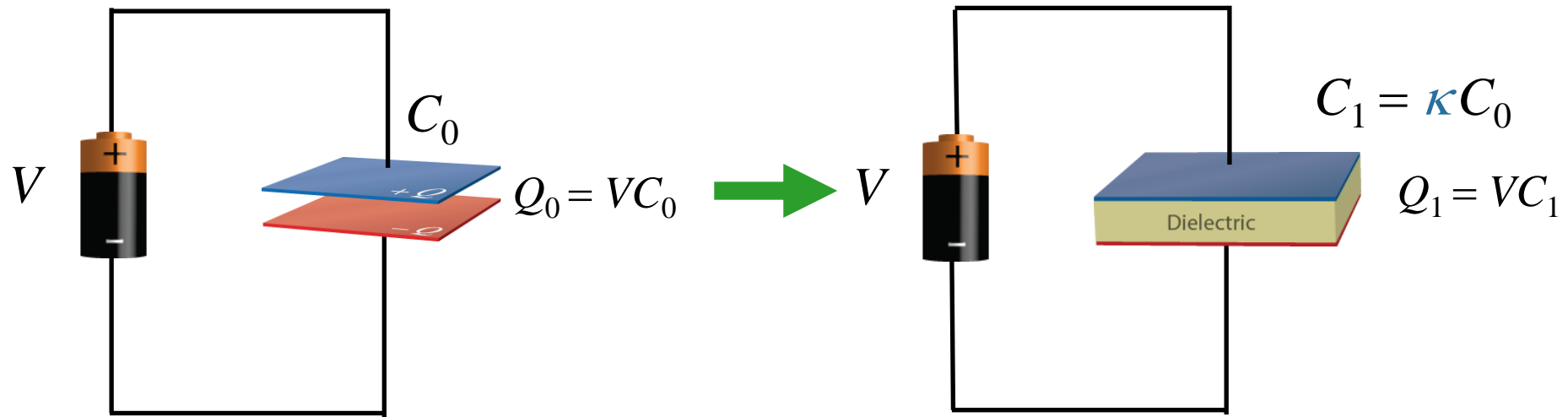

By adding a dielectric, you are just making a new capacitor with larger capacitance (factor of  $\kappa$ )
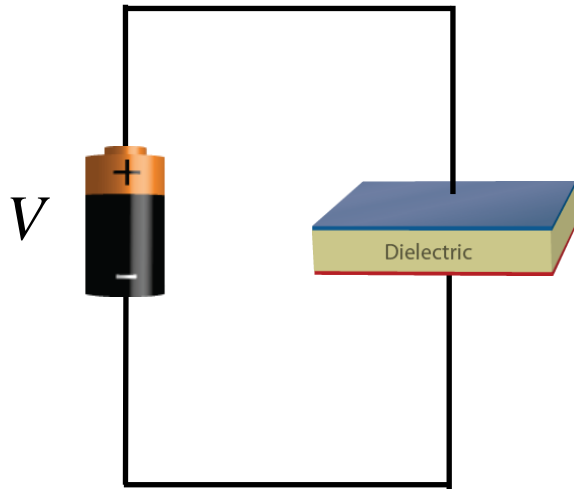
# Messing with Capacitors

If connected to a battery  $V$  stays constant




$$V_1 = V$$

$$C_1 = \kappa C$$

$$\left. \begin{array}{l} V_1 = V \\ C_1 = \kappa C \end{array} \right\} \rightarrow Q_1 = C_1 V_1$$

$$= \kappa C V = \kappa Q$$

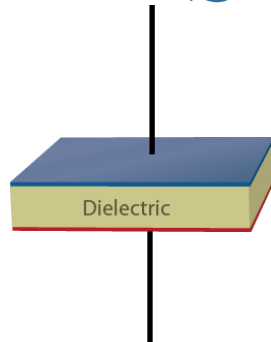If isolated, then total  $Q$  stays constant



$$Q_1 = Q$$

$$C_1 = \kappa C$$


$$\left. \begin{array}{l} Q_1 = Q \\ C_1 = \kappa C \end{array} \right\} \rightarrow V_1 = Q_1 / C_1$$

$$= Q / \kappa C = V / \kappa$$
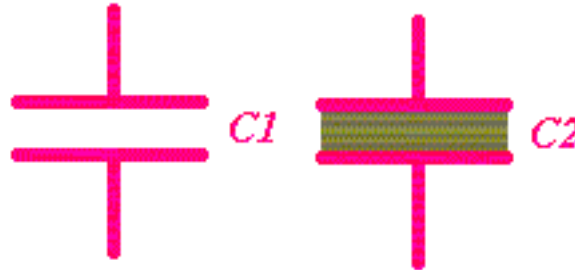
# Check Point 4a



Two identical parallel plate capacitors are given the same charge  $Q$ , after which they are disconnected from the battery. Then, a dielectric is placed between the plates of  $C_2$



Compare the voltages of the two capacitors.



**A**  $V_1 > V_2$    **B**  $V_1 = V_2$    **C**  $V_1 < V_2$

" $Q$  is constant,  $C$  increases,  $C = Q/V$ ."
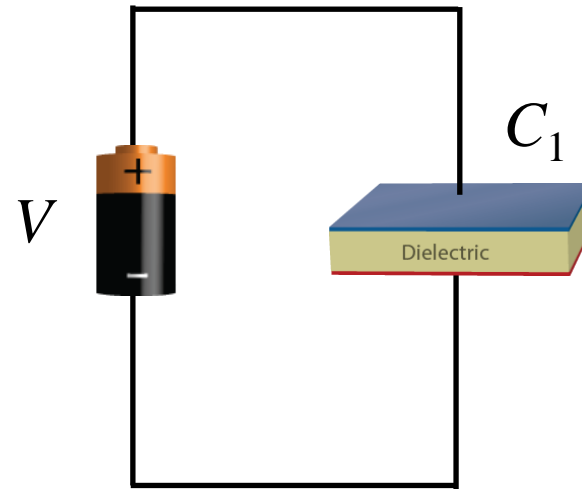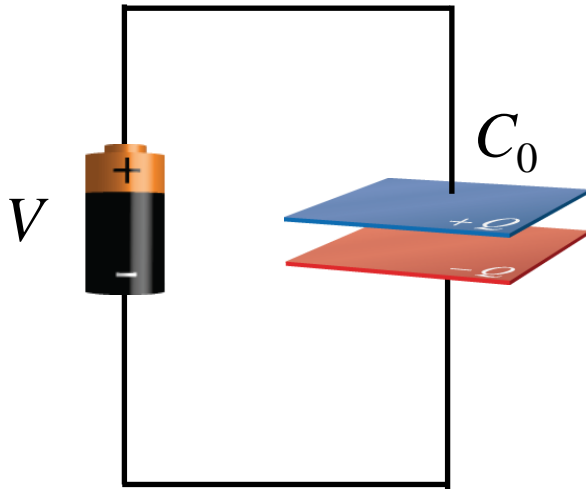
# Messing with Capacitors Clicker Question



Two identical parallel plate capacitors are connected to identical batteries. Then a dielectric is inserted between the plates of capacitor  $C_1$ . Compare the energy stored in the two capacitors.



A)  $U_1 < U_0$

B)  $U_0 = U_1$

C)  $U_1 > U_0$

Compare using  $U = \frac{1}{2}CV^2$


$$U_1/U_0 = \kappa$$

→ Potential Energy goes UP
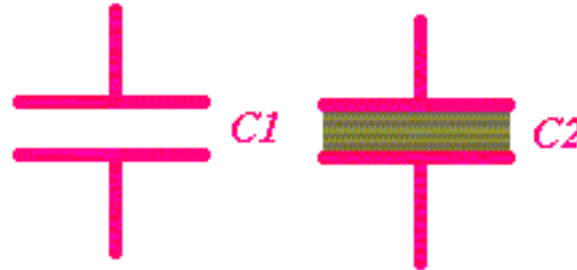
# CheckPoint 4b



Two identical parallel plate capacitors are given the same charge  $Q$ , after which they are disconnected from the battery. Then, a dielectric is placed between the plates of  $C_2$




Compare the potential energy stored by the two capacitors.

- A)  $U_1 > U_2$    B)  $U_1 = U_2$    C)  $U_1 < U_2$
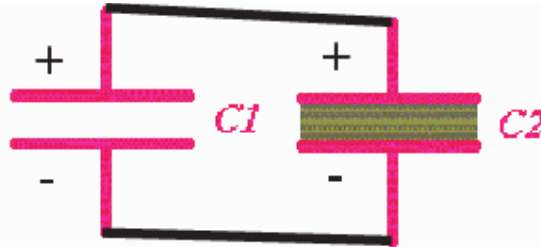
# Checkpoint 4c



Two identical parallel plate capacitors are given the same charge  $Q$ , after which they are disconnected from the battery. After  $C_2$  has been charged and disconnected, it is filled with a dielectric. **The two capacitors are now connected to each other by wires as shown. How will the charge redistribute itself, if at all?**




- A. The charges will flow so that the charge on  $C_1$  will become equal to the charge on  $C_2$ .
- B. The charges will flow so that the energy stored in  $C_1$  will become equal to the energy stored in  $C_2$ .
- C. The charges will flow so that the potential difference across  $C_1$  will become the same as the potential difference across  $C_2$ .
- D. No charges will flow. The charge on the capacitors will remain what it was before they were connected.

**$V$  must be the same !!**

$$Q: \quad \frac{Q_1}{C_1} = \frac{Q_2}{C_2} \quad \longrightarrow \quad Q_1 = \frac{C_1}{C_2} Q_2$$

$$U: \quad \begin{aligned} U_1 &= \frac{1}{2} C_1 V^2 \\ U_2 &= \frac{1}{2} C_2 V^2 \end{aligned} \quad \longrightarrow \quad U_1 = \frac{C_1}{C_2} U_2$$

# Calculation

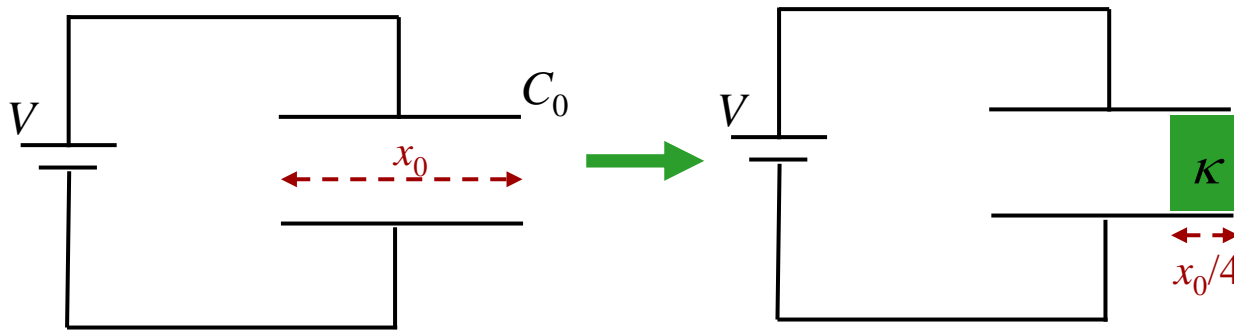

An air-gap capacitor, having capacitance  $C_0$  and width  $x_0$  is connected to a battery of voltage  $V$ .

A dielectric ( $\kappa$ ) of width  $x_0/4$  is inserted into the gap as shown.

What is  $Q_f$ , the final charge on the capacitor?

Conceptual Analysis:

$$C \equiv \frac{Q}{V}$$

What changes when the dielectric added?

- A) Only  $C$     B) only  $Q$     C) only  $V$     D)  $C$  and  $Q$     E)  $C$  and  $V$

Adding dielectric changes the physical capacitor


→  $C$  changes

$V$  does not change and  $C$  changes

→  $Q$  changes



# Calculation

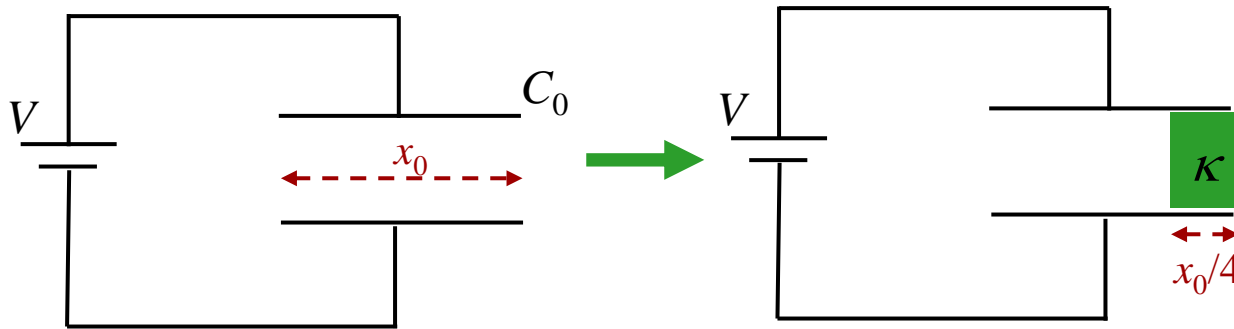

An air-gap capacitor, having capacitance  $C_0$  and width  $x_0$  is connected to a battery of voltage  $V$ .

A dielectric ( $\kappa$ ) of width  $x_0/4$  is inserted into the gap as shown.

## Strategic Analysis:

- Calculate new capacitance  $C$
- Apply definition of capacitance to determine  $Q$

To calculate  $C$ , let's first look at:




- A)  $V_{left} < V_{right}$     B)  $V_{left} = V_{right}$     C)  $V_{left} > V_{right}$

The conducting plate is an equipotential !

What is  $Q_f$ , the final charge on the capacitor?

# Calculation

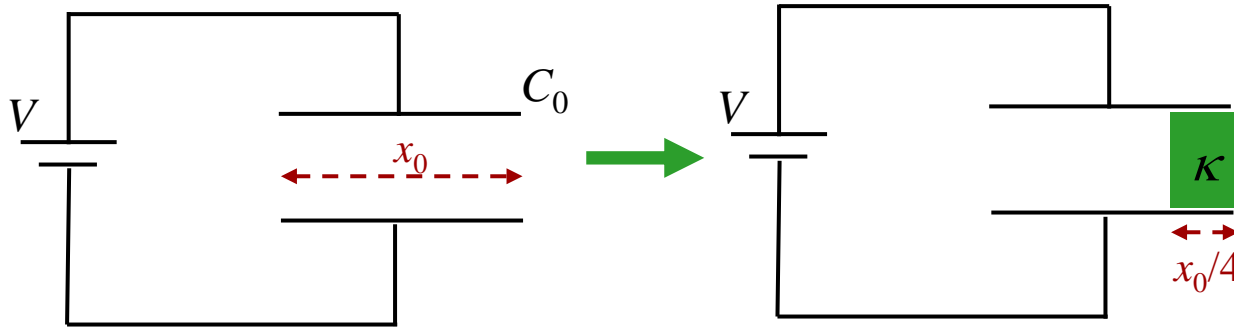


An air-gap capacitor, having capacitance  $C_0$  and width  $x_0$  is connected to a battery of voltage  $V$ .

A dielectric ( $\kappa$ ) of width  $x_0/4$  is inserted into the gap as shown.

What is  $Q_f$ , the final charge on the capacitor?

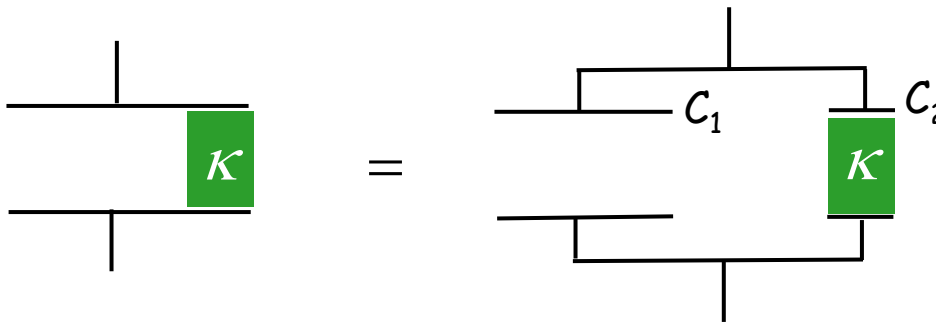
Can consider capacitor to be two capacitances,  $C_1$  and  $C_2$ , in parallel



What is  $C_1$  ?

- A)  $C_1 = C_0$    B)  $C_1 = \frac{3}{4}C_0$    C)  $C_1 = \frac{4}{3}C_0$    D)  $C_1 = \frac{9}{16}C_0$

# Calculation

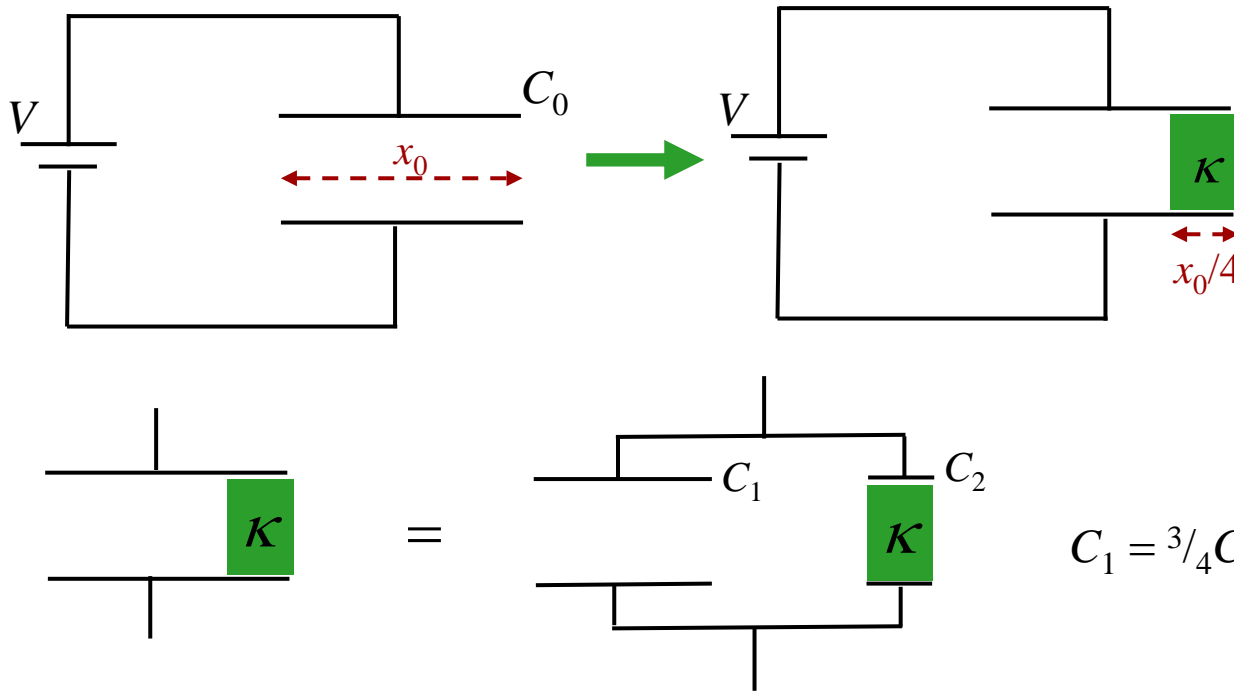

An air-gap capacitor, having capacitance  $C_0$  and width  $x_0$  is connected to a battery of voltage  $V$ .

A dielectric ( $\kappa$ ) of width  $x_0/4$  is inserted into the gap as shown.


What is  $Q_f$ , the final charge on the capacitor?

What is  $C_2$  ?

- A)  $C_2 = \kappa C_0$     B)  $C_2 = \frac{3}{4} \kappa C_0$     C)  $C_2 = \frac{4}{3} \kappa C_0$     **D)  $C_2 = \frac{1}{4} \kappa C_0$**

In general. For parallel plate capacitor filled with dielectric:  $C = \kappa \epsilon_0 A/d$

# Calculation

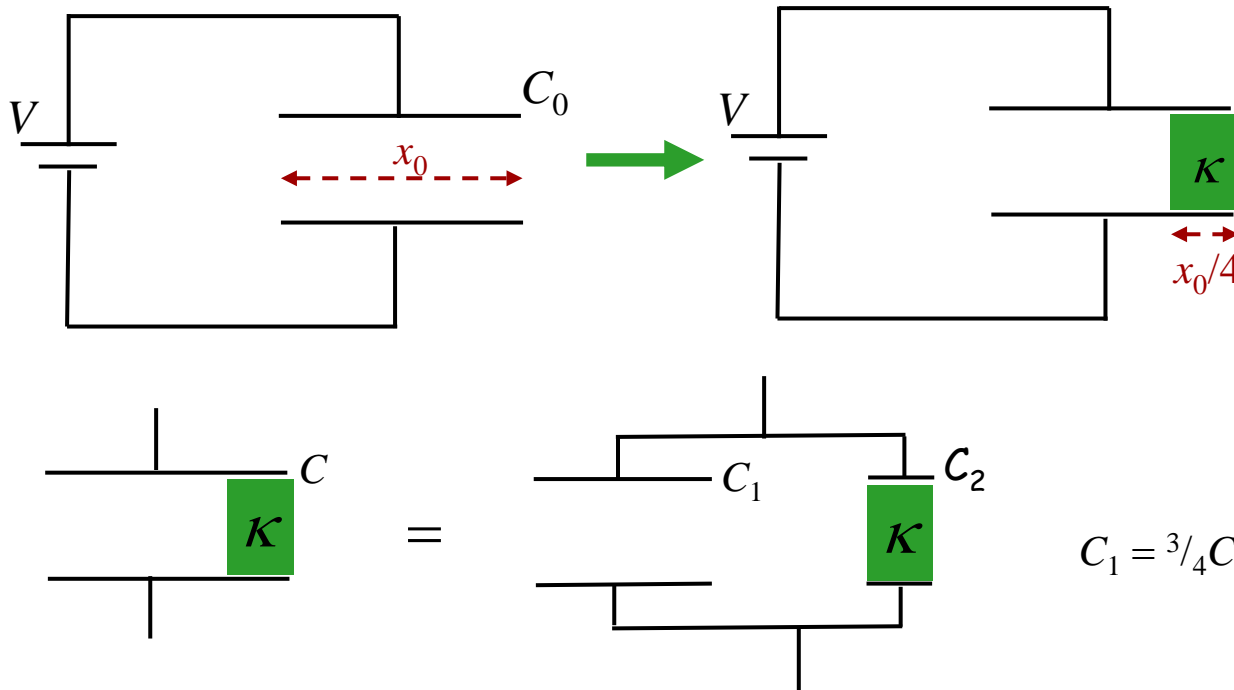

An air-gap capacitor, having capacitance  $C_0$  and width  $x_0$  is connected to a battery of voltage  $V$ .

A dielectric ( $\kappa$ ) of width  $x_0/4$  is inserted into the gap as shown.

What is  $Q_f$ , the final charge on the capacitor?

$$C_1 = \frac{3}{4}C_0$$

$$C_2 = \frac{1}{4}\kappa C_0$$

What is  $C$ ?


A)  $C = C_1 + C_2$     B)

C)  $C = \left( \frac{1}{C_1} + \frac{1}{C_2} \right)^{-1}$

$C$  = parallel combination of  $C_1$  and  $C_2$ :  $C = C_1 + C_2$


$\rightarrow C = C_0 \left( \frac{3}{4} + \frac{1}{4}\kappa \right)$

# Calculation

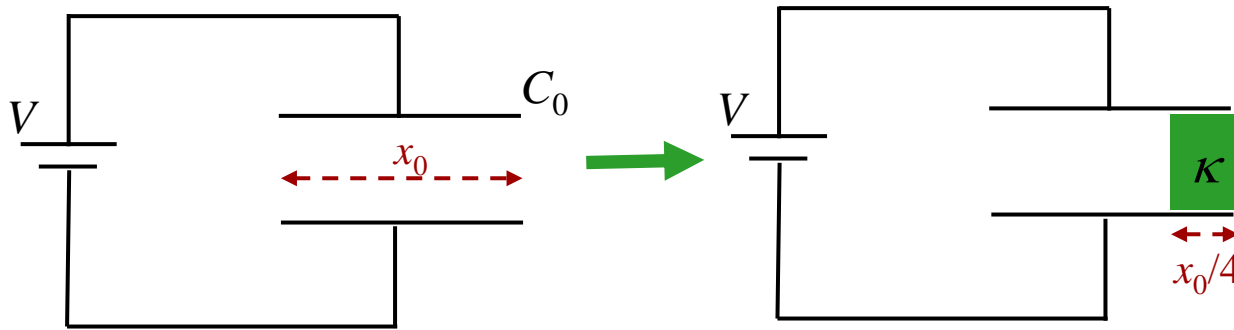

An air-gap capacitor, having capacitance  $C_0$  and width  $x_0$  is connected to a battery of voltage  $V$ .

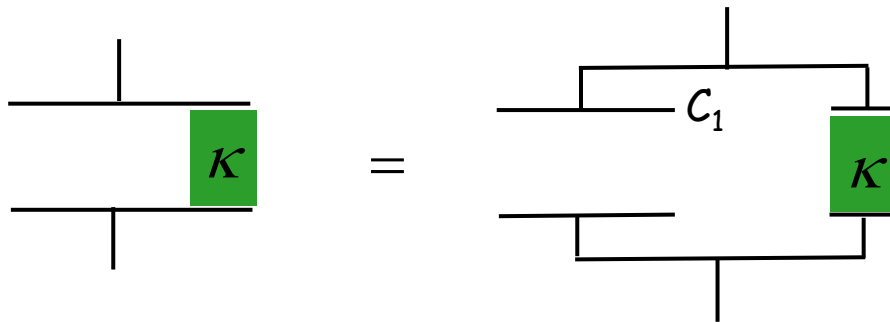A dielectric ( $\kappa$ ) of width  $x_0/4$  is inserted into the gap as shown.



What is  $Q_f$ , the final charge on the capacitor?

$$C_1 = \frac{3}{4}C_0$$

$$C_2 = \frac{1}{4}\kappa C_0$$

$$\rightarrow C = C_0 \left( \frac{3}{4} + \frac{1}{4}\kappa \right)$$

What is  $Q$ ?

$$C \equiv \frac{Q}{V} \rightarrow Q = VC$$

$$Q_f = VC_0 \left( \frac{3}{4} + \frac{1}{4}\kappa \right)$$